 


RISC V Microarchitecture

Dr. Girish H
Professor
Department of ECE
Cambridge Institute of Technology
&
Kavinesh
Research Staff
CCCIR
Cambridge Institute of Technology


Microarchitecture

- Introduction
- Single-Cycle Processor



Introduction

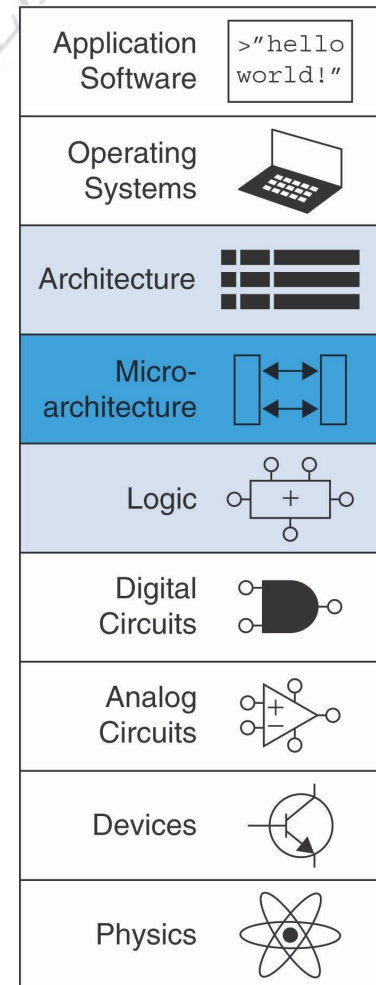- **Microarchitecture:** how to implement an architecture in hardware
- Processor:
 - **Datapath:** functional blocks
 - **Control:** control signals



Microarchitecture

- Multiple implementations for a single architecture:
 - **Single-cycle:** Each instruction executes in a single cycle
 - **Multicycle:** Each instruction is broken up into series of shorter steps
 - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once

Processor

Performance

- Program execution time

Execution Time =

$(\text{\#instructions})(\text{cycles/instruction})(\text{seconds/cycle})$

- **Definitions:**
 - CPI: Cycles/instruction
 - clock period: seconds/cycle
 - IPC: instructions/cycle = IPC
- **Challenge is to satisfy constraints of:**
 - Cost
 - Power
 - Performance

RISC-V Processor

- Consider **subset** of RISC-V instructions:
 - R-type instructions:
 - **add, sub, and, or, slt**
 - I-type instruction:
 - **lw**
 - S-type instruction:
 - **sw**
 - B-type instructions:
 - **beq**


Architectural State Elements

Determines everything about a processor:

- Architectural state:

- 32 registers
- PC
- Memory

RISC-V Architectural State Elements

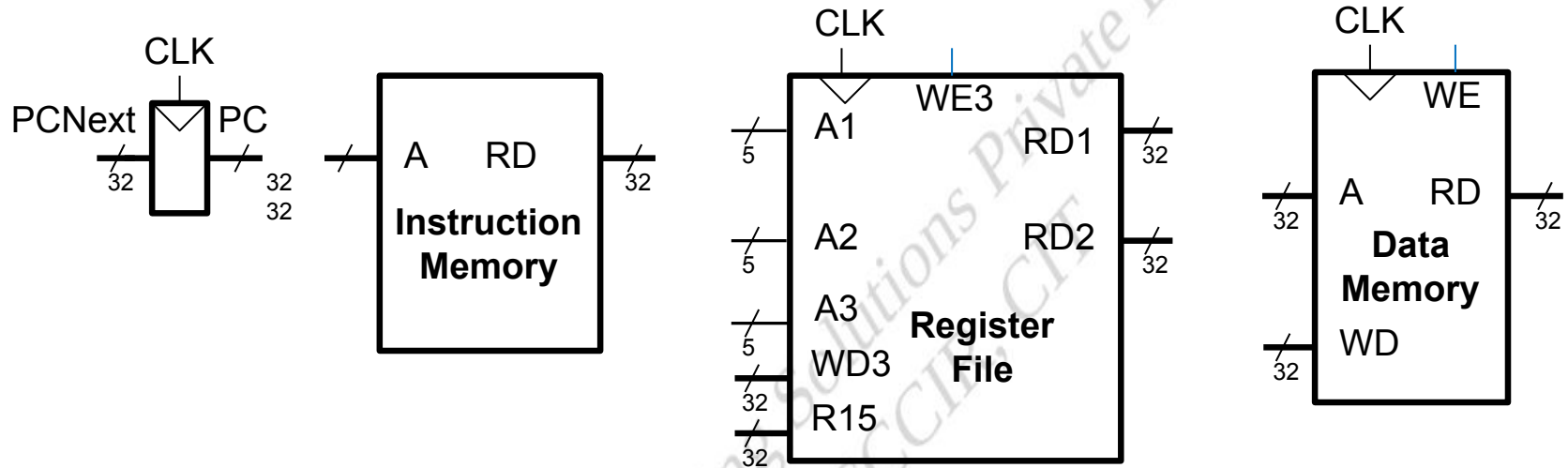

Single-Cycle RISC-V Processor

- Datapath
- Control


Single-Cycle RISC-V Processor

- **Datapath**
- Control


RISC-V Processor

- **R-type instructions:**
 - **add, sub, and, or, slt**
- **I-type instruction:**
 - **lw**
- **S-type instruction:**
 - **sw**
- **B-type instructions:**
 - **beq**


R-Type

 


I-Type

 


S-Type

 

B-Type

 

Single-Cycle RISC-V Datapath

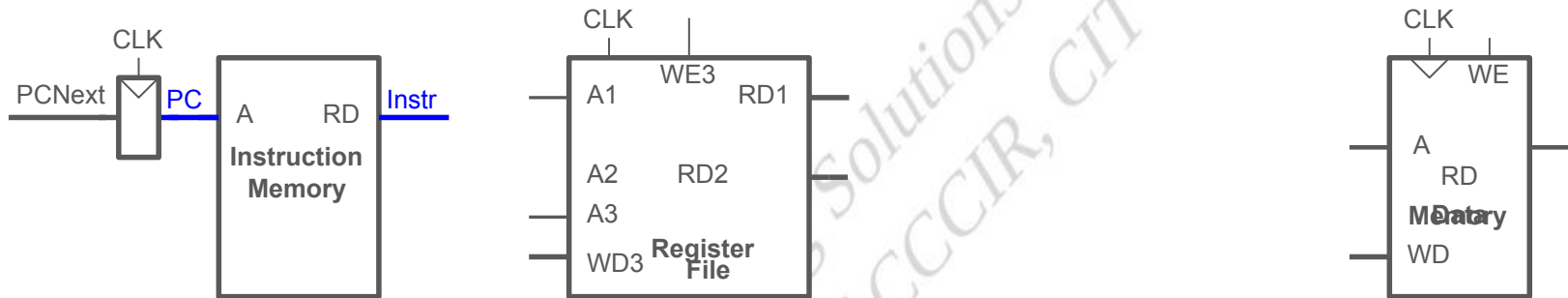


Single-Cycle RISC-V Processor

- **Datapath:** start with `lw`

instruction `lw t2, -8(s3)`


- **Example:** `lw rd, imm(rs1)`

I-Type

 

Single-Cycle Datapath: $1w$ fetch


STEP 1: Fetch instruction

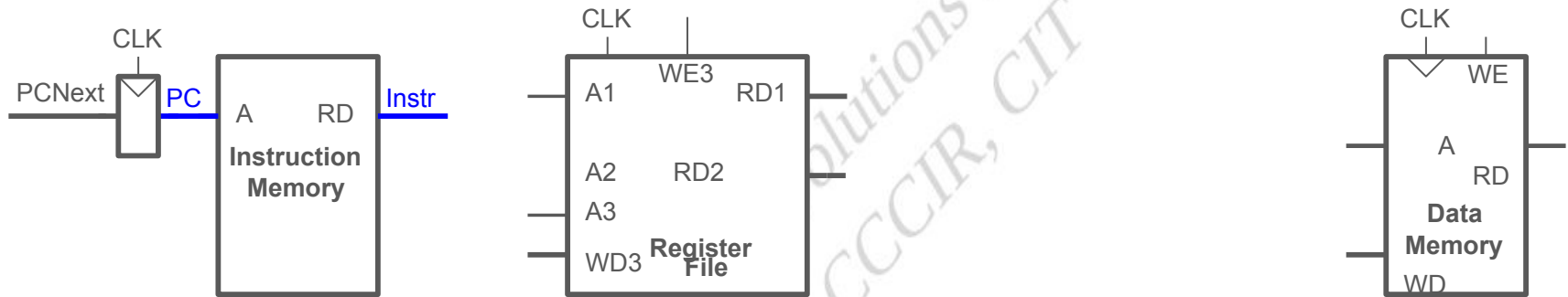


Single-Cycle Datapath: lw Reg

Read

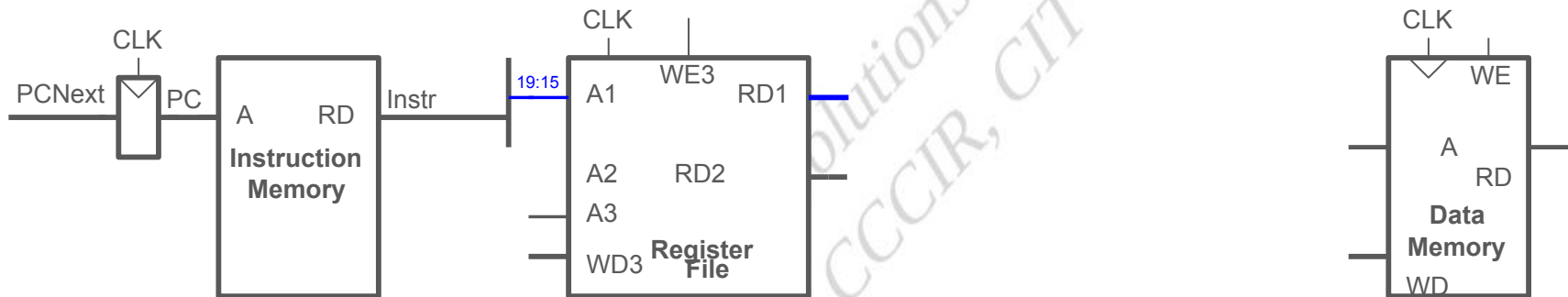STEP 2: Read source operand (**rs1**) from RF



I-Type

 


lw rd, imm(rs1)

Single-Cycle Datapath: $1w$

Immediate


STEP 3: Extend the immediate

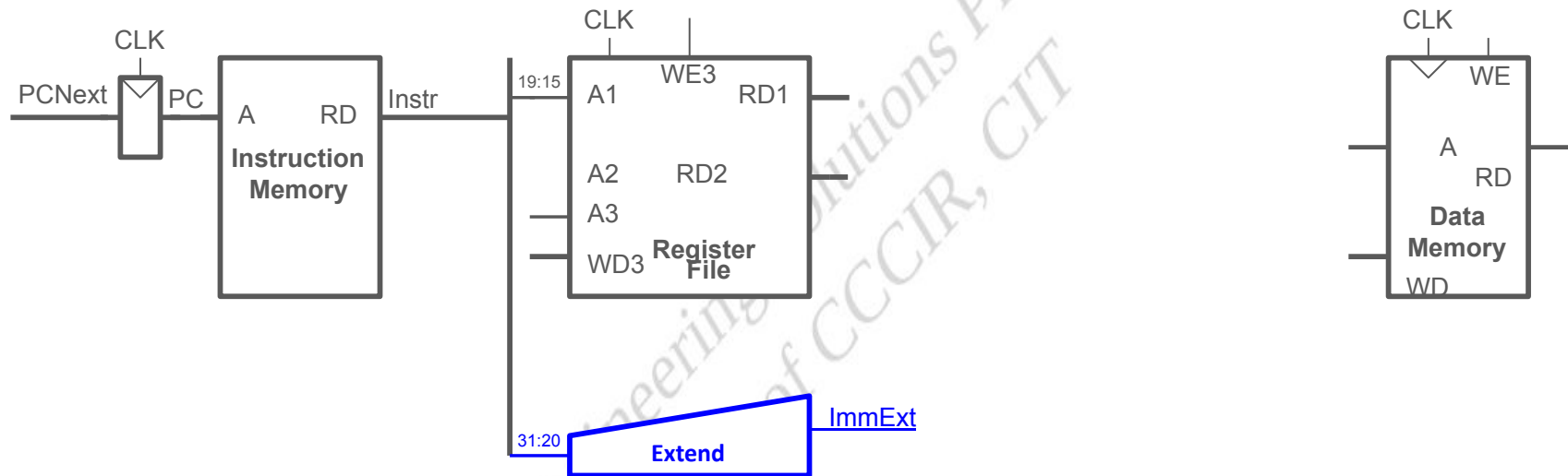

Single-Cycle Datapath: $1w$

Address


STEP 4: Compute the memory address

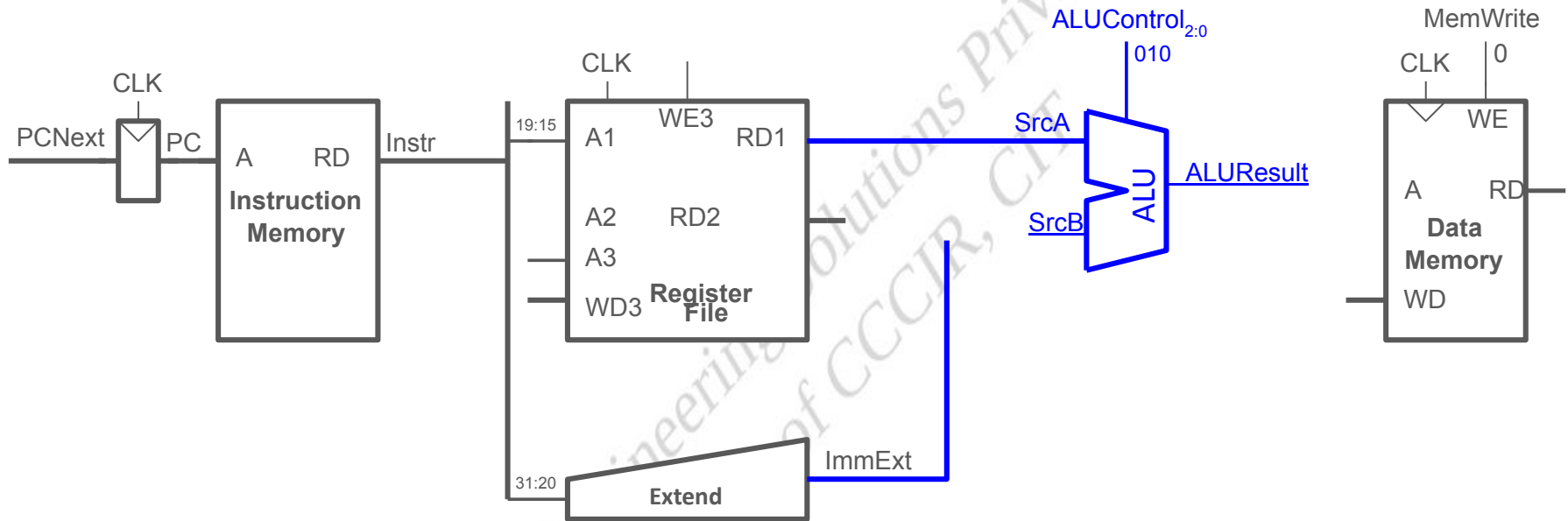

Single-Cycle Datapath: LDR Mem


Read

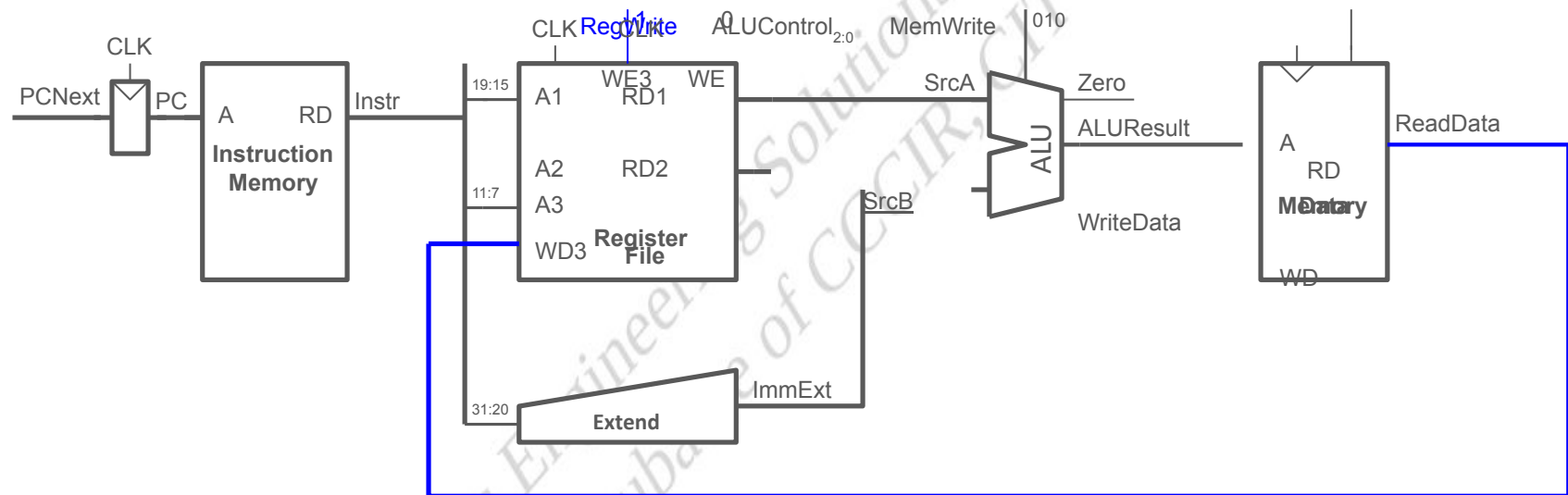STEP 5: Read data from memory and write it back to register file



Single-Cycle Datapath: PC Increment

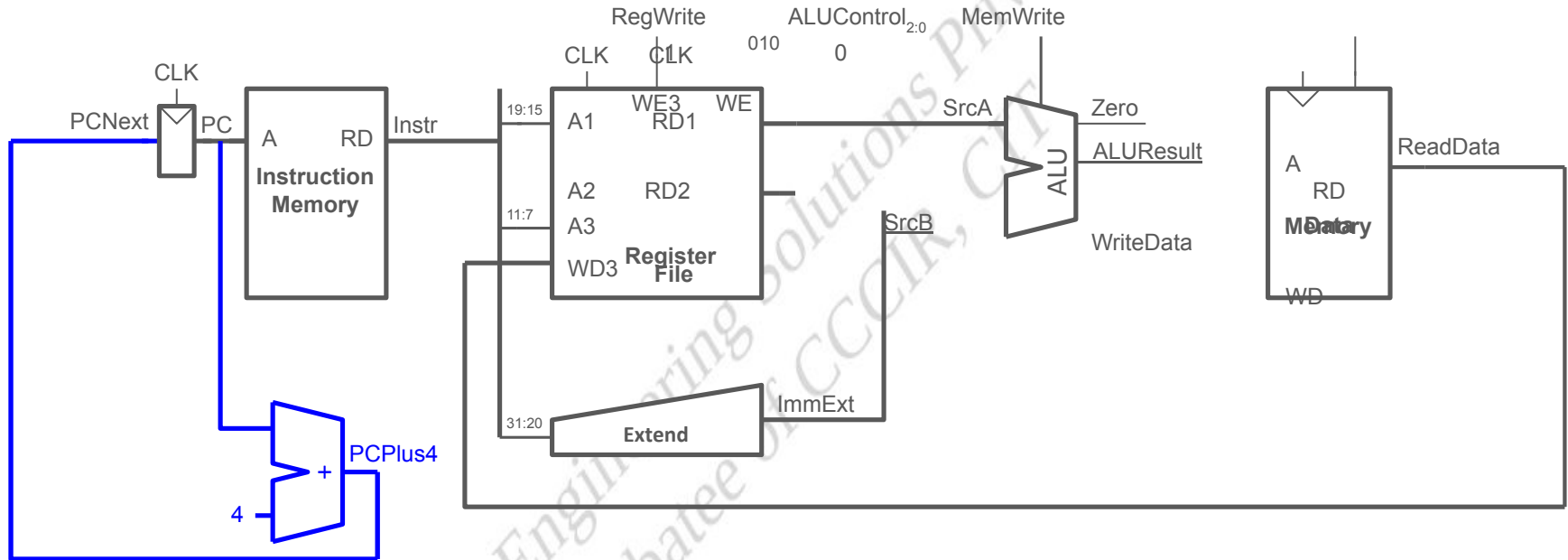STEP 6: Determine address of next instruction




Single-Cycle Datapath: sw


Expand datapath to handle sw :

- Write data in $rs2$ to memory
- **Example:** $sw\ t2,\ 0xc(s3)$
 $sw\ rs2,\ imm(rs1)$

S-Type

 

 - **Immediate:** now in {instr[31:25], instr[11:7]}
- **Add control signals:** ImmSrc, MemWrite




sw rs2, imm(rs1)


Single-Cycle Datapath: Immediate

ImmSrc	ImmExt	Instruction Type
0	{{20{instr[31]}}, instr[31:20]}	I-Type
1	{{20{instr[31]}}, instr[31:25], instr[11:7]}	S-Type

I-Type

 

S-Type

 


Single-Cycle Datapath:

R-Type

- **Instructions:** add, sub, and, or, slt,

- **Example:** add s1, s2, s3
 op rd, rs1, rs2


R-Type

 

Single-Cycle Datapath:

R-Type

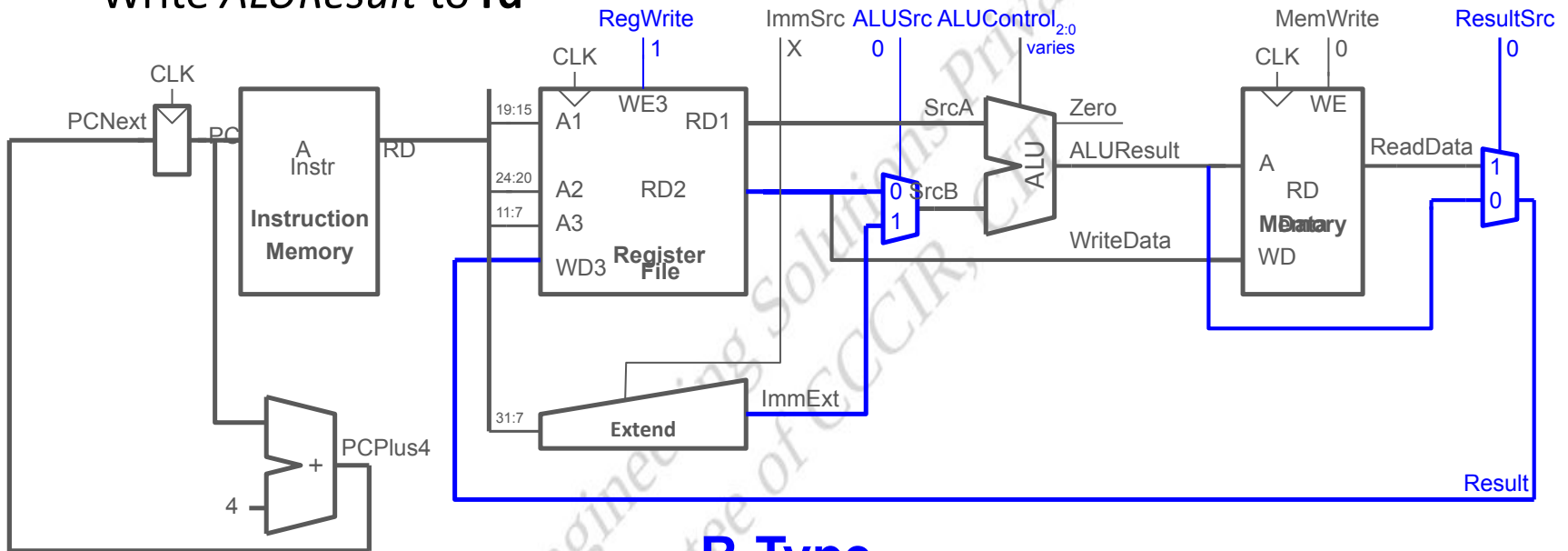- Read from **rs1** and **rs2** (instead of **imm**)
- Write **ALUResult** to **rd**




R-Type

31:25	24:20	19:15	14:12	11:7	6:0
funct7	rs2	rs1	funct3	rd	op
7 bits	5 bits	5 bits	3 bits	5 bits	7 bits


add rd, rs1, rs2

Single-Cycle Datapath: beq

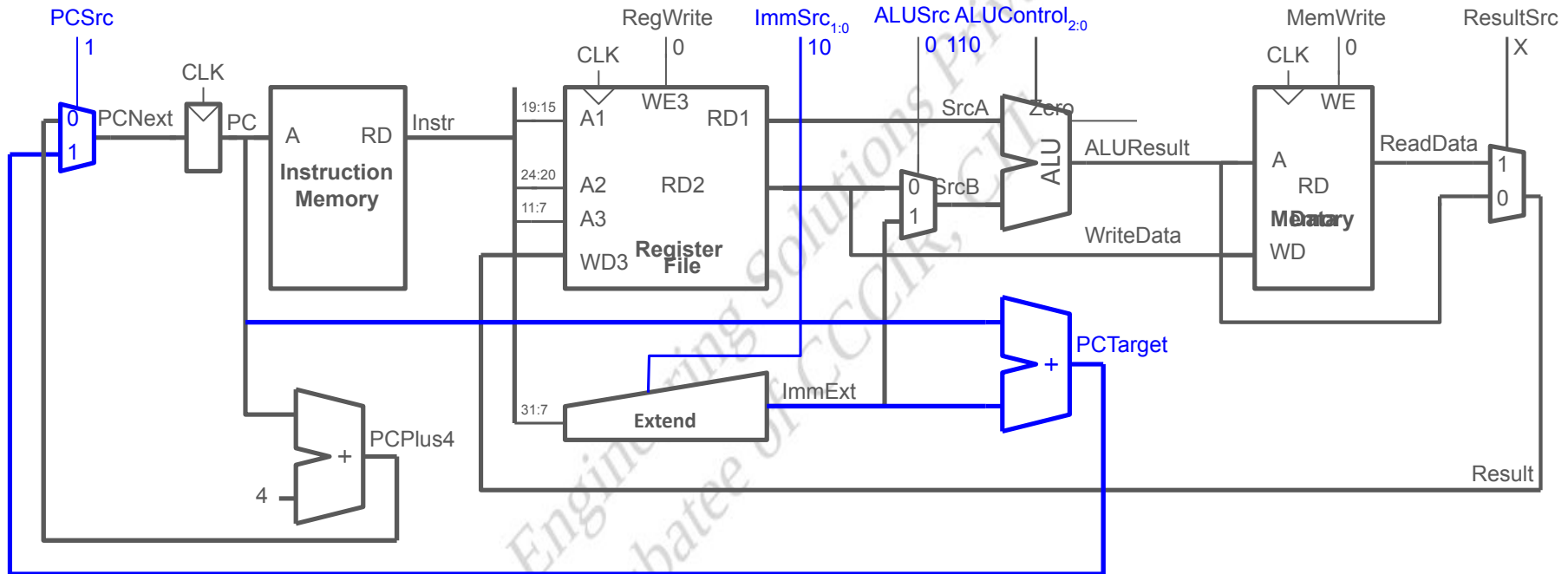Calculate branch target address: $PCTarget = PC + imm$



B-Type

 

`beq rs1, rs2, Label`


Single-Cycle Datapath: ImmExt

ImmSrc _{1:0}	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20]}	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7]}	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0}	B-Type


I-Type




S-Type

 


B-Type

 

Single-Cycle RISC-V Processor

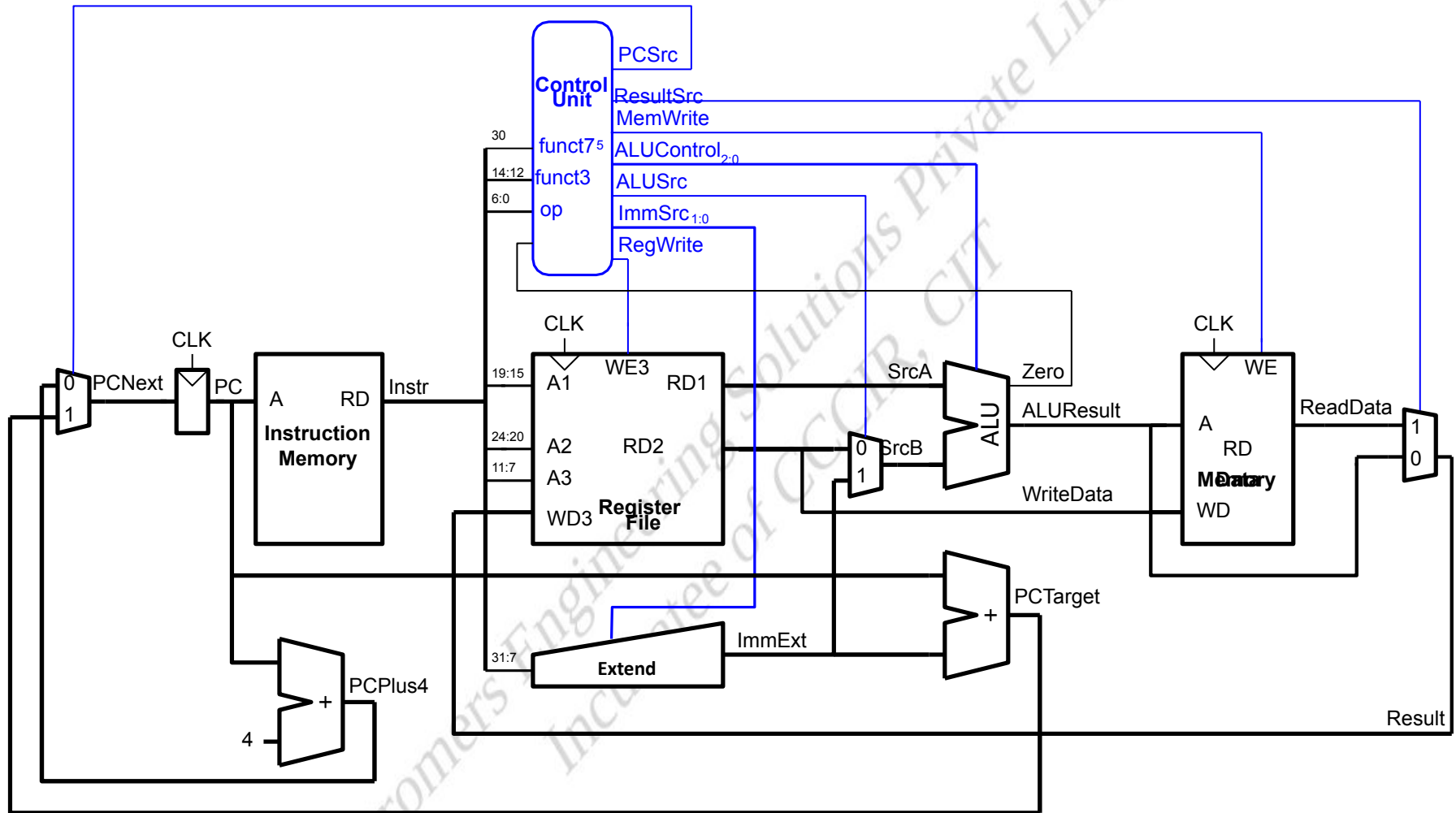


Single-Cycle Control

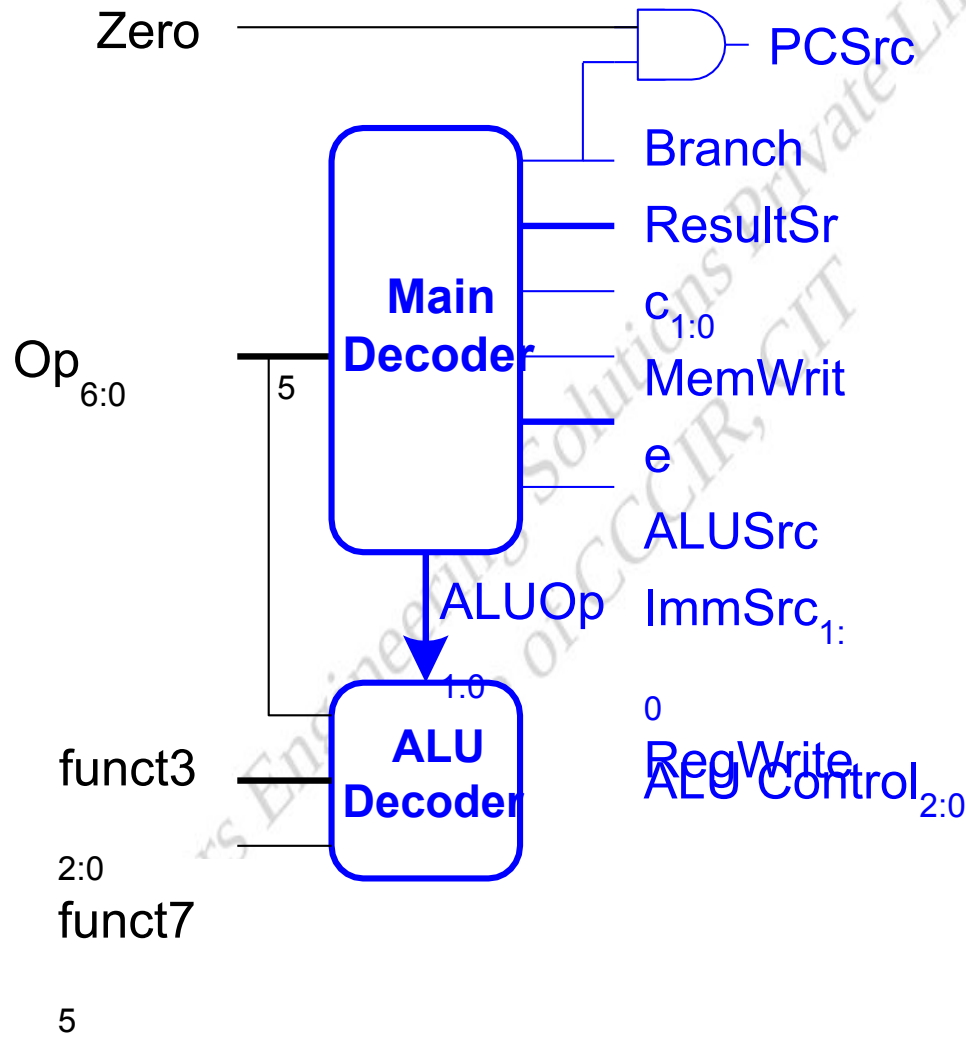


Control Unit: Main Decoder

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	lw	1	00	1	0	1	0	00
35	sw	0	01	1	1	X	0	00
51	R-type	1	XX	0	0	0	0	10
99	beq	0	10	0	0	X	1	01

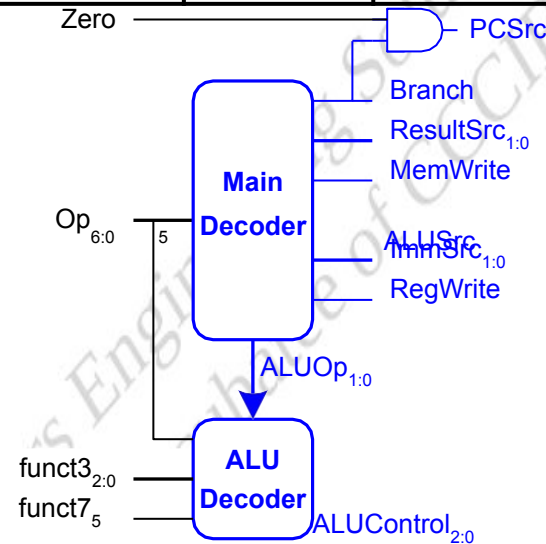


Review: ALU

 


ALUControl _{2:0}	Function
000	A & B
001	A B
010	A + B
110	A - B
111	SLT

Review: ALU

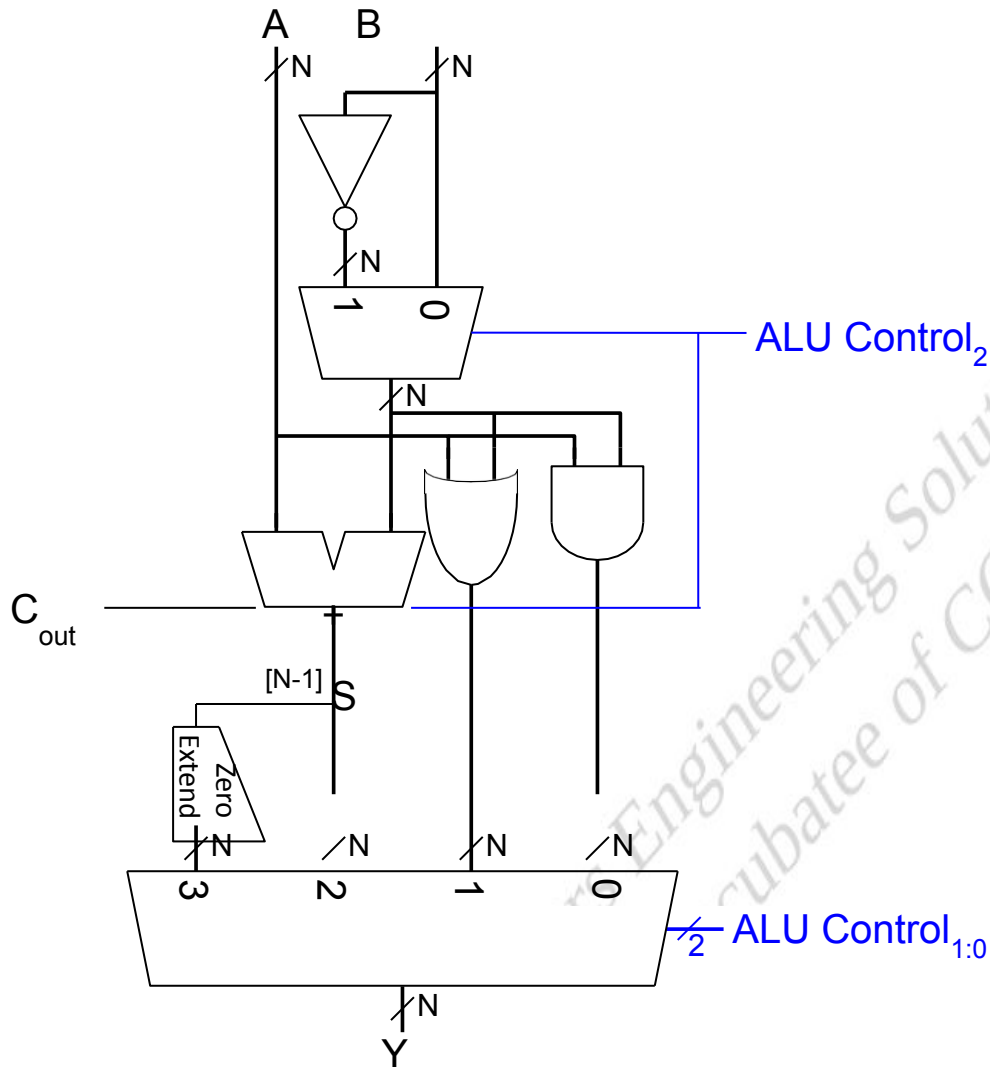


ALU Control _{2:0}	Function
000	A & B
001	A B
010	A + B
110	A - B
111	SLT

Single-Cycle Control: ALU Decoder

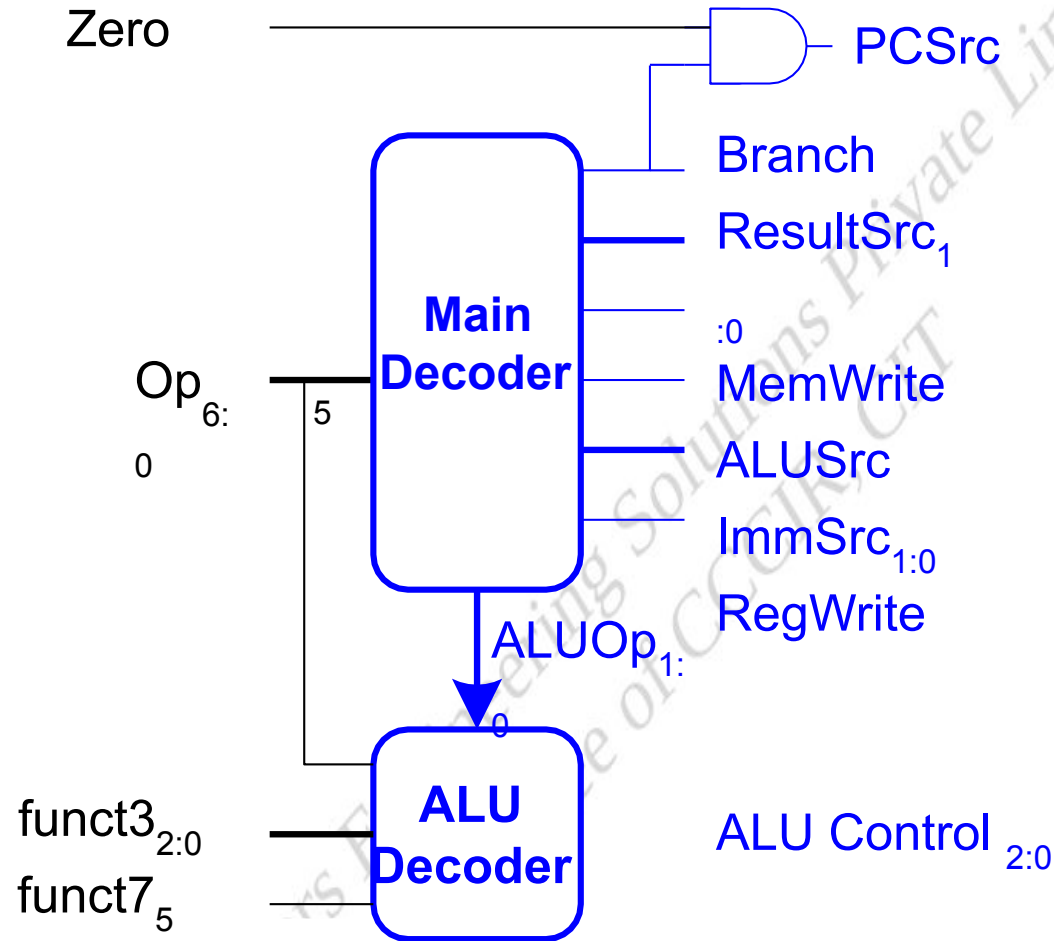


Control Unit: ALU Decoder

ALUOp	op ₅	funct3	funct7 ₅	Instruction	ALUControl _{2:0}
00	X	X	X	lw, sw	010 (add)
01	X	X	X	beq	110 (subtract)
10	X	000	0	add	010 (add)
	1	000	1	sub	110 (subtract)
	X	010	0	slt	111 (set less than)
	X	110	0	or	001 (or)
	X	111	0	slt	000 (and)

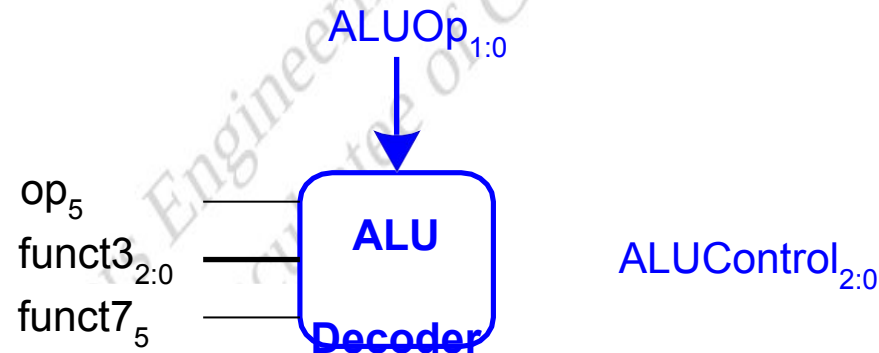


Example: or

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
51	R-type	1	XX	0	0	0	0	10

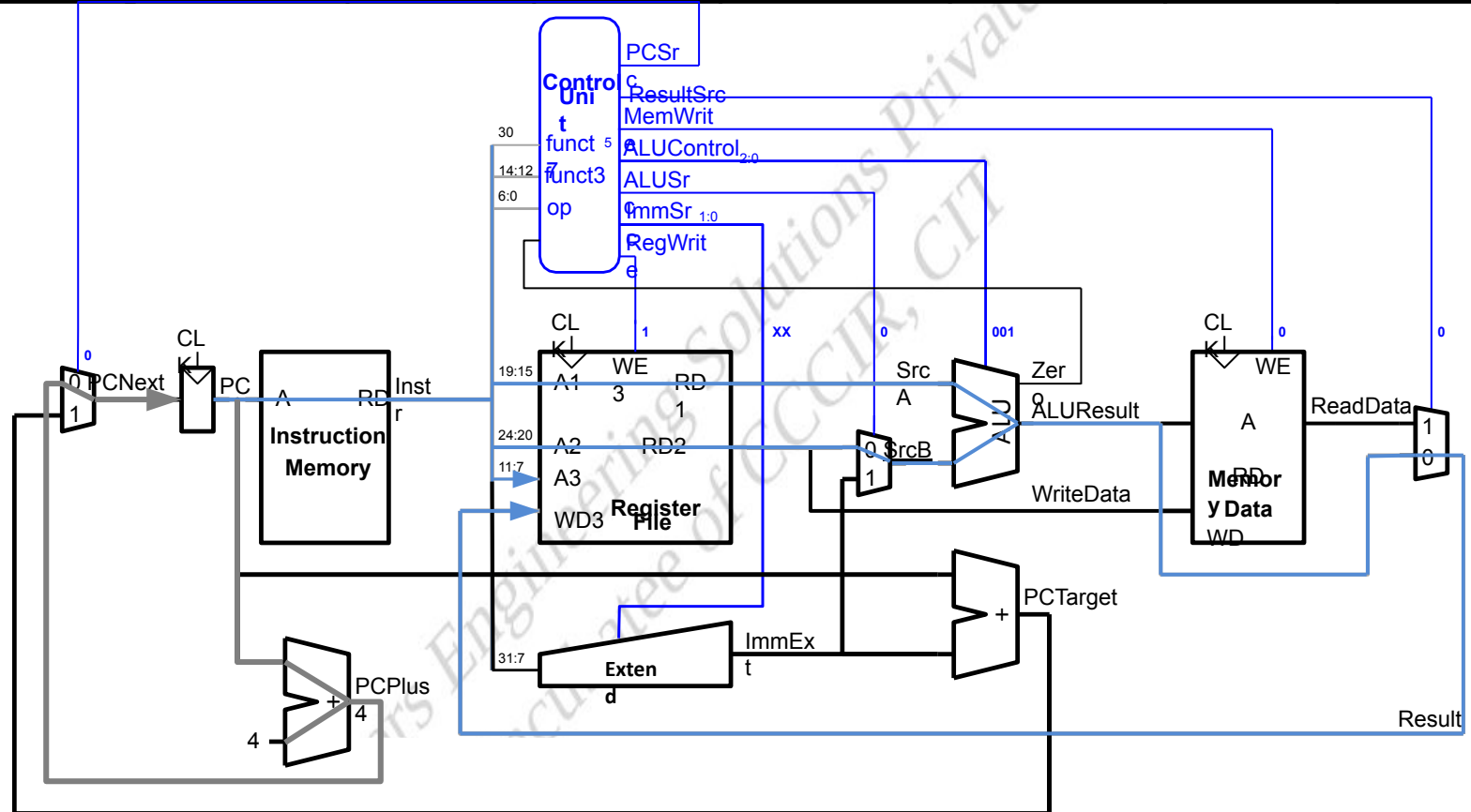

Example: or

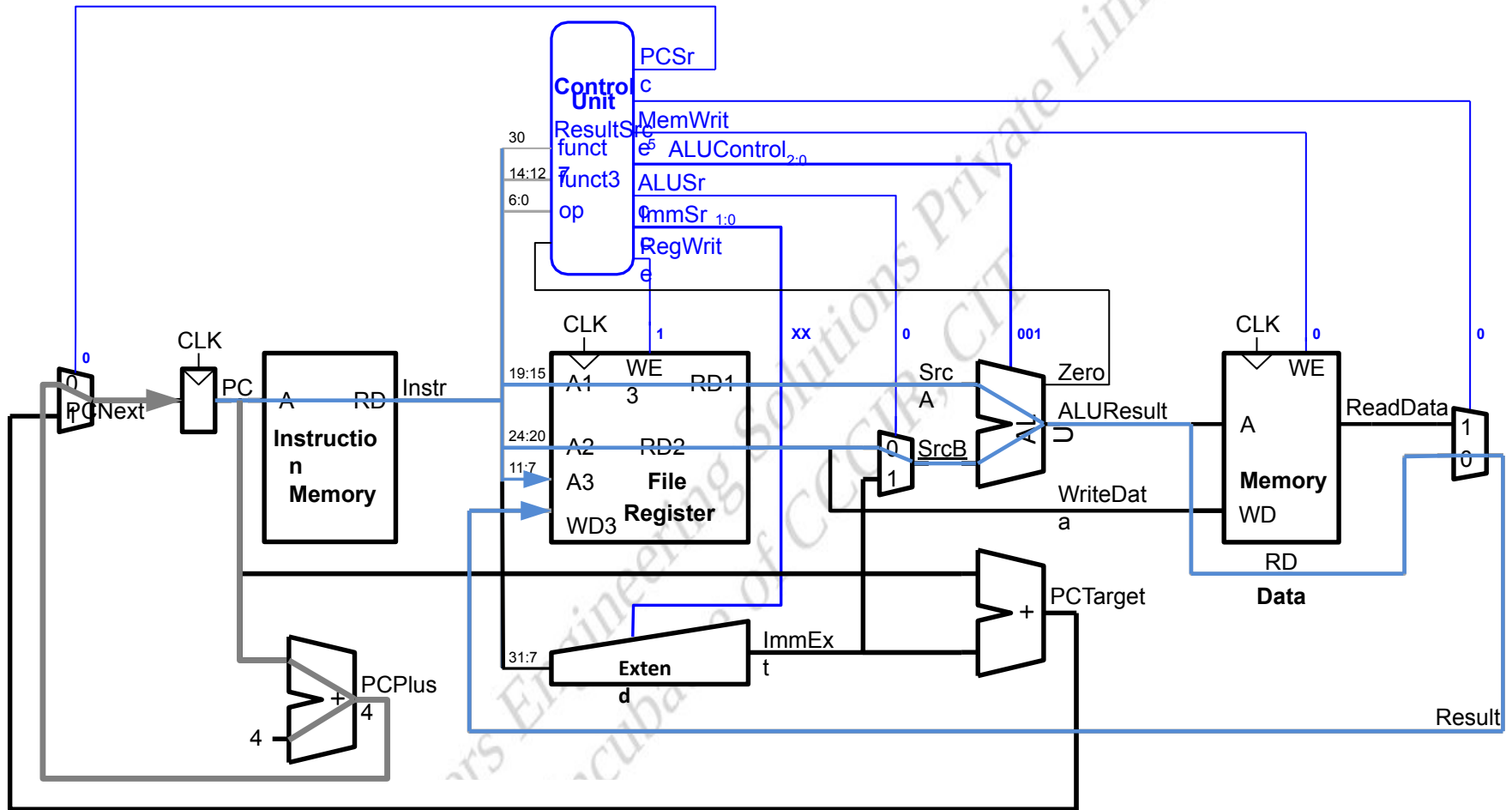


Extended Functionality: addi


op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	lw	1	00	1	0	1	0	00
35	sw	0	01	1	1	X	0	00
51	R-type	1	XX	0	0	0	0	10
99	beq	0	10	0	0	X	1	01
19	addi	1	00	1	0	0	0	10

Extended Functionality: addi

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
19	addi	1	00	1	0	0	0	10

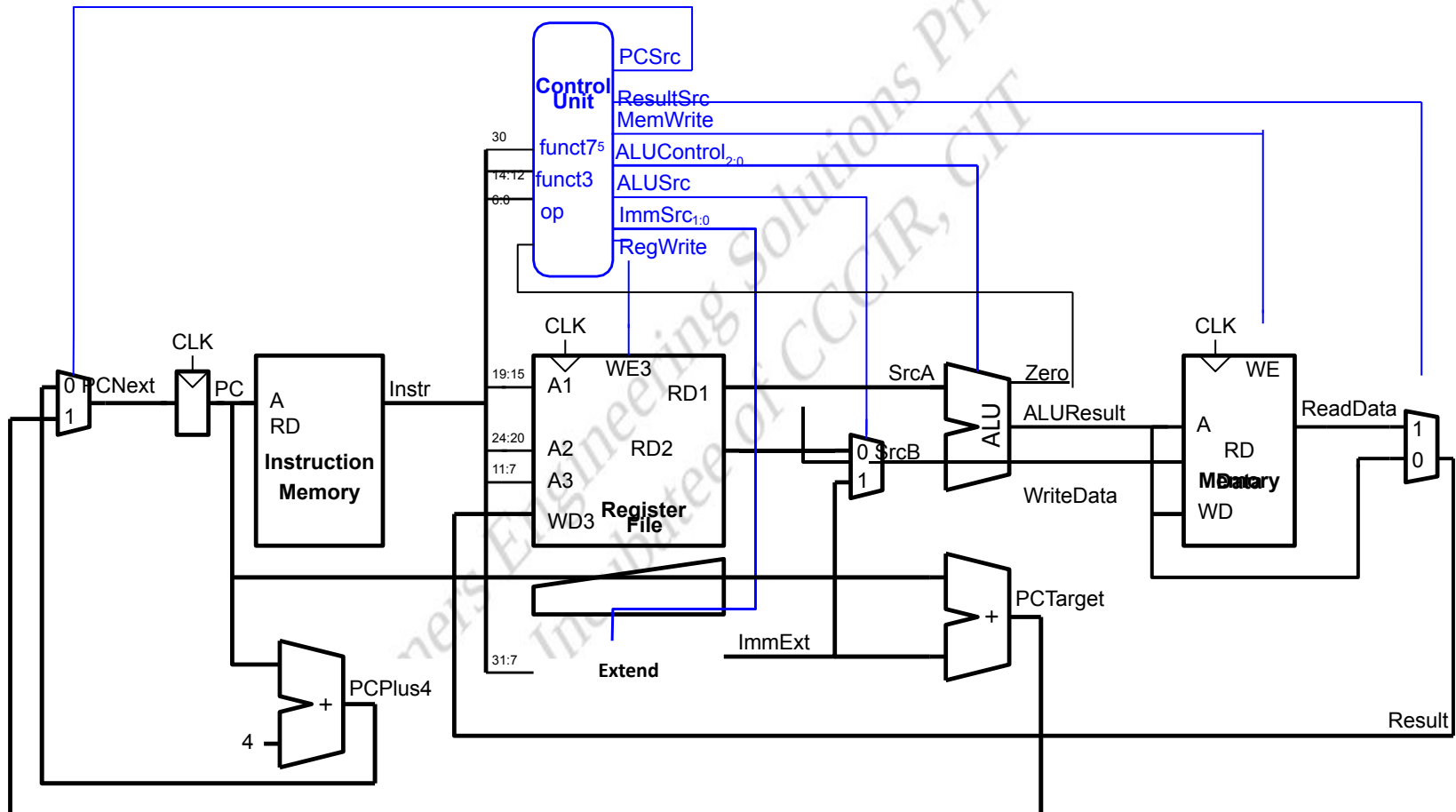


Extended Functionality: jal

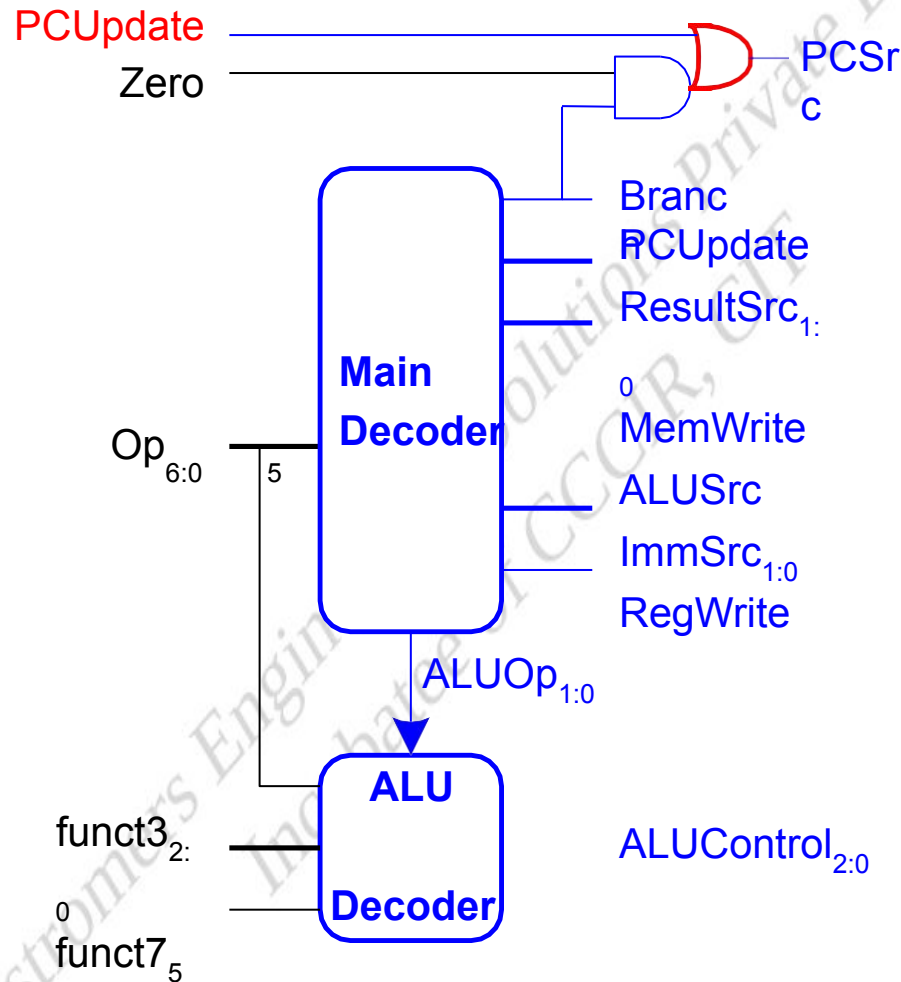


Single-Cycle Datapath: ImmExt

ImmSrc _{1:0}	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20]}	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7]}	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0}	B-Type
11	{{12{instr[31]}}, instr[19:12], instr[20], instr[30:21], 1'b0}	J-Type


I-Type

 

B-Type

 

S-Type

 

J-Type



Extended Functionality: jal

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	PCUpdate
3	lw	1	00	1	0	10	0	00	0
35	sw	0	01	1	1	XX	0	00	0
51	R-type	1	XX	0	0	01	0	10	0
99	beq	0	10	0	0	XX	1	01	0
19	addi	1	00	1	0	01	0	10	0
111	jal	0	11	X	0	00	0	XX	1

Extended Functionality: jal

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	PCUpdate
111	jal	0	11	X	0	00	0	XX	1

